

Astables RC à AOP

Exercice 1

1. On a deux seuils de basculement : $v^+ = \pm V_{sat} \frac{R_1}{R_1 + R_2}$


$$V_1 = 11V \times 10 / (10+10)$$

$$V_1 = 5,5V$$

$$V_2 = -10,5V \times 10 / (10+10)$$

$$V_2 = -5,25V$$

2.

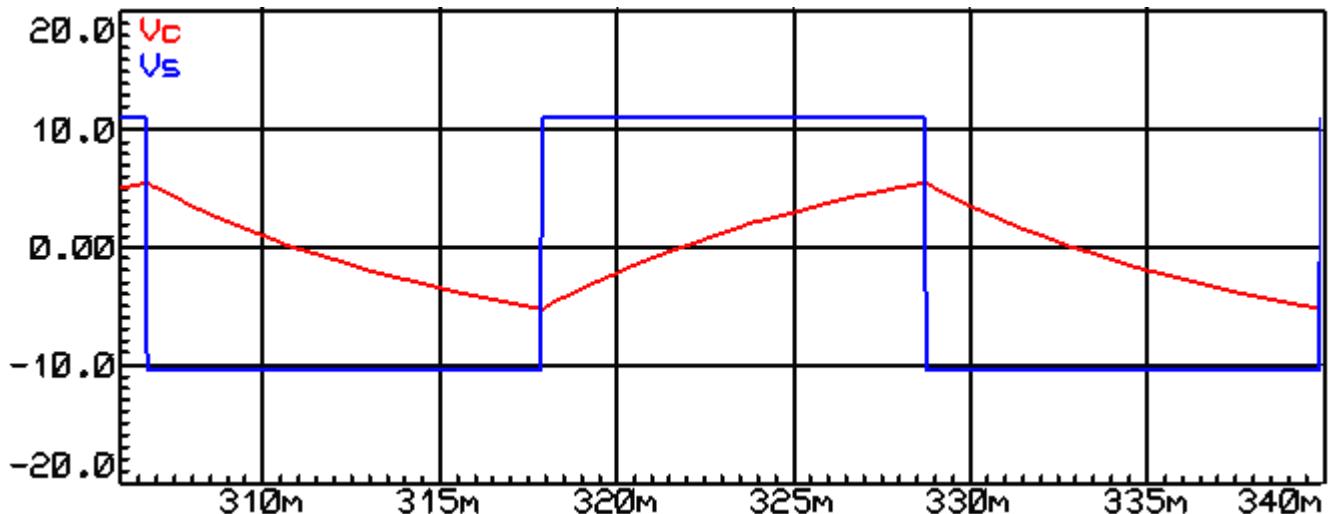

3.

$$V_H = +V_{sat} = 11V$$

$$V_B = -V_{sat} = -10,5V$$

$$V_1 = 5,5V$$

$$V_2 = -5,25V$$

$$t_H = RCL \ln \frac{V_H - V_2}{V_H - V_1}$$

$$t_H = 10 \cdot 10^3 \cdot 10^{-6} \ln [(11 - (-5,25)) / (11 - 5,5)]$$

$$t_H = 10,83ms$$

$$t_B = RCL \ln \frac{V_B - V_1}{V_B - V_2}$$

$$t_B = 10 \cdot 10^3 \cdot 10^{-6} \ln [(-10,5 - 5,5) / (-10,5 - (-5,25))]$$

$$t_B = 11,14ms$$

$$T = t_H + t_B = 10,83ms + 11,14ms$$

$$T = 21,97 \approx 22ms$$

Exercice 2

- 1.** La diode D_1 permet la charge du condensateur à travers la résistance R_1 lorsque $V_s = +V_{sat}$.

La diode D_2 permet la décharge du condensateur dans la résistance R_2 lorsque $V_s = -V_{sat}$.

- 2.** On a deux seuils de basculement : $v+ = \pm V_{sat} \frac{R_3}{R_3 + R_4}$

$$V_1 = 11V \times 2,2 / (2,2 + 2,2)$$

$$\boxed{V_1 = 5,5V}$$

$$V_2 = -10,5V \times 2,2 / (2,2 + 2,2)$$

$$\boxed{V_2 = -5,25V}$$

3. $V_H = +V_{sat} - V_D = 11V - 0,6V = 10,4V$

$$V_B = -V_{sat} + V_D = -10,5V + 0,6V = -9,9V$$

$$V_1 = -5,25V \quad V_2 = +5,5V$$

$$t_H = RCL \ln \frac{V_H - V_2}{V_H - V_1}$$

$$t_H = 3,3 \cdot 10^3 \cdot 10^{-6} \ln [(10,4 - (-5,25)) / (10,4 - 5,5)]$$

$$\boxed{t_H = 3,83ms}$$

$$t_B = RCL \ln \frac{V_B - V_1}{V_B - V_2}$$

$$t_B = 4,7 \cdot 10^3 \cdot 10^{-6} \ln [(-9,9 - 5,5) / (-9,9 - (-5,25))]$$

$$\boxed{t_B = 5,63ms}$$

$$T = t_H + t_B = 3,83ms + 5,63ms$$

$$\boxed{T = 9,46ms \approx 9,5ms}$$

4. $\alpha = t_H / (t_H + t_B) = 3,83ms / 9,46ms$

$$\boxed{\alpha = 0,4}$$

- 5.** $V_s = \pm V_{sat}$, qui dépend de l'alimentation de l'AOP. Donc l'amplitude maximale de V_s dépend de l'alimentation de l'AOP.

Exercice 3

1. On a deux seuils de basculement :

$$v+ = \pm V_{sat} \frac{R_1}{R_1 + R_2} \quad \text{et} \quad \pm V_{sat} = \pm (V_Z + V_D) = \pm (4,7V + 0,6V) = \pm 5,3V$$

$$V_1 = 5,3V \times 1,2 / (1,2 + 2,2)$$

$$V_1 = 1,87V$$

$$V_2 = -5,3V \times 1,2 / (1,2 + 2,2)$$

$$V_2 = -1,87V$$

2. $V_H = +V_{sat} = 5,3V \quad V_B = -V_{sat} = -5,3V$

$$t_H = 3,3 \cdot 10^3 \cdot 10^{-6} \ln [(5,3 - (-1,87)) / (5,3 - 1,87)]$$

$$t_H = 2,43ms$$

$$t_B = 3,3 \cdot 10^3 \cdot 10^{-6} \ln [(-5,3 - 1,87) / (-5,3 - (-1,87))]$$

$$t_B = 2,43ms$$


$$T = t_H + t_B = 2 \times 2,43ms$$

$$T = 4,86ms \approx 5ms$$

3. $\alpha = t_H / (t_H + t_B) = t_H / 2t_H$

$$\alpha = 0,5$$

4.

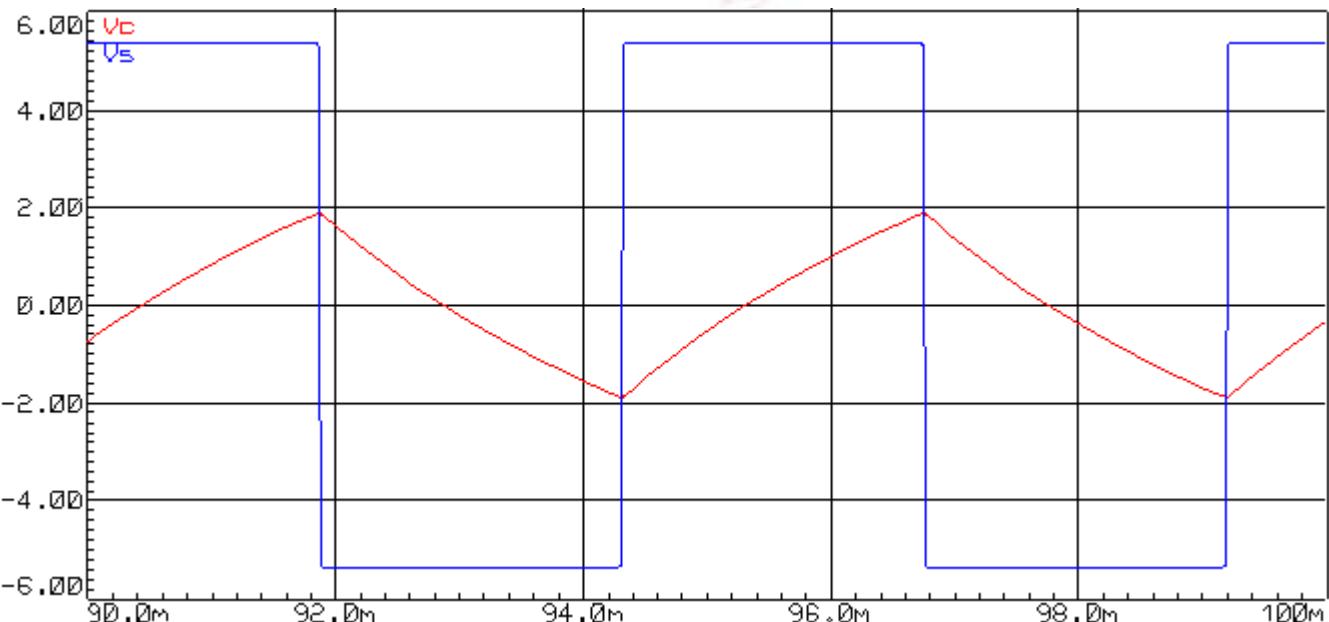

Exercice 4

$$1. \quad v+ = \frac{\frac{V_{cc}}{R_3} + \frac{V_s}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \text{ et} \quad V_s = \pm V_{sat} \quad +V_{sat} = V_{cc} = 5V \quad -V_{sat} = 0V$$

On a deux seuils de basculement :

$$V_1 = \frac{\frac{V_{cc}}{R_3} + \frac{V_{cc}}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{5V}{15} + \frac{5V}{1,2}}{\frac{1}{3,3} + \frac{1}{1,2} + \frac{1}{15}}$$

$$V_1 = 3,74V$$

$$V_2 = \frac{\frac{V_{cc}}{R_3} + \frac{0}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{5V}{15}}{\frac{1}{3,3} + \frac{1}{1,2} + \frac{1}{15}}$$

$$V_2 = 0,28V$$

$$2. \quad V_H = +V_{sat} = 5V \quad V_B = -V_{sat} = 0V$$

$$t_H = 3,3 \cdot 10^3 \cdot 10^{-6} \ln [(5 - 0,28)/(5 - 3,74)] \quad t_H = 4,36ms$$

$$t_B = 3,3 \cdot 10^3 \cdot 10^{-6} \ln [(0 - 3,74)/(0 - 0,28)] \quad t_B = 8,55ms$$

$$T = t_H + t_B = 4,36ms + 8,55ms \quad T = 12,91ms \approx 13ms$$

$$3. \quad \alpha = t_H / (t_H + t_B) = t_H / T \quad \alpha \approx 0,34$$

4.

